
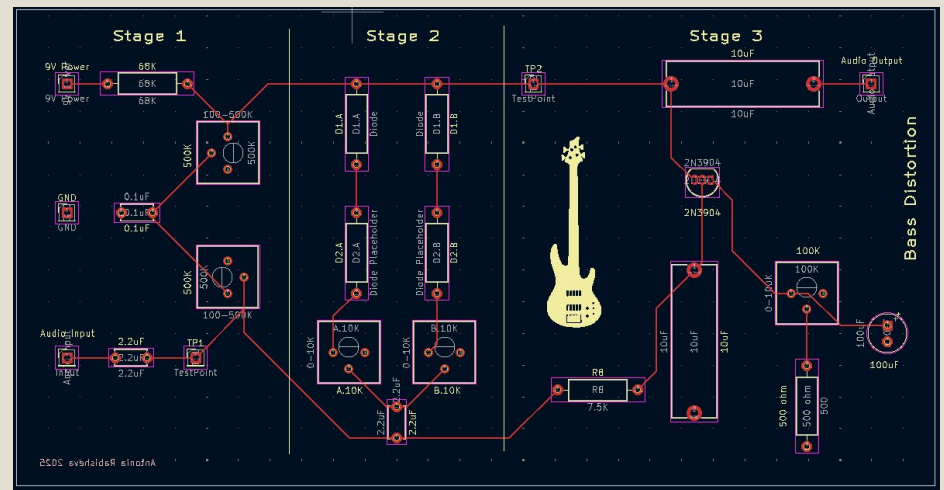


MPI Lead: Toni

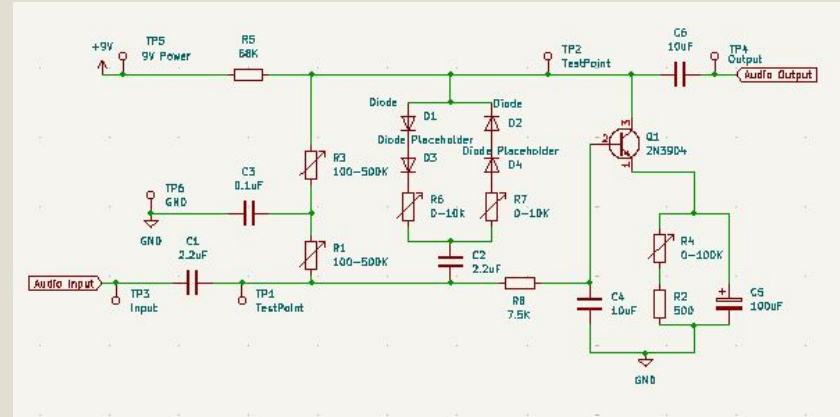


Transistors in Analog Design

Bass Distortion





Audio Amplifier	A circuit that increases the amplitude of low-power audio signals to a level suitable for driving loudspeakers, usually including filters in their design for better sound reproduction
Filter	A circuit that selectively allows signals of certain frequencies to pass while attenuating others. It's commonly used to remove unwanted noise or to separate different frequency components in a signal
Amplification vs Switching	In BJT transistors, amplification occurs when the transistor operates in the active region , where it linearly increases the input signal's amplitude . In contrast, switching uses the transistor in either cutoff (off) or saturation (on) regions, acting like an electronic on/off switch rather than varying signal strength.
AC vs DC	AC (Alternating Current) is a signal that constantly changes direction and varies in voltage over time , often forming a wave-like shape such as a sine wave. DC (Direct Current) is a flat, constant signal that stays at the same voltage level
DC Offset	Refers to biasing of transistors → A constant DC voltage needs to be set and applied to the base to ensure the transistor operates within the correct region (active in our case)
Clipping	Clipping , in relation to diodes, occurs when diodes are used in a circuit to limit the voltage of a signal by cutting off (or "clipping") parts of the waveform that exceed certain voltage levels . This creates a flattened top or bottom of the signal
Feedback	Feedback in a BJT transistor circuit involves routing a portion of the output signal back to the input to influence the transistor's behavior . Can be negative or positive.

Terminology & Concepts

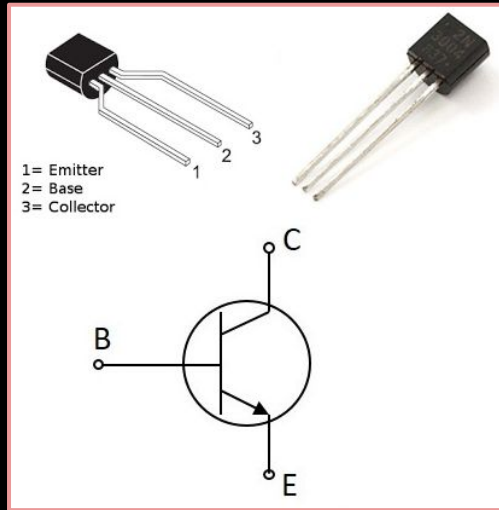

NPN BJT Transistor

AC and DC Signals

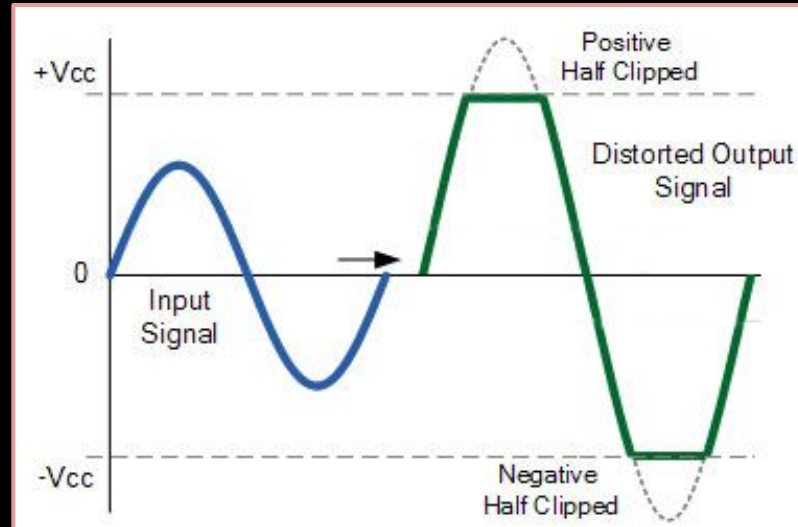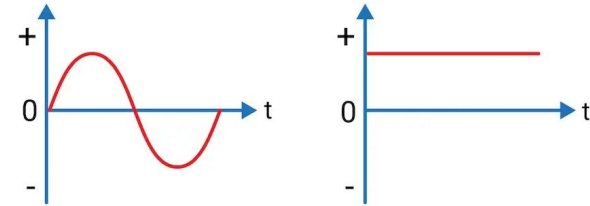

Clipping


TRIM POT 10K Ω



1 2 3

Wiper contact

FUNCTIONAL DIAGRAM

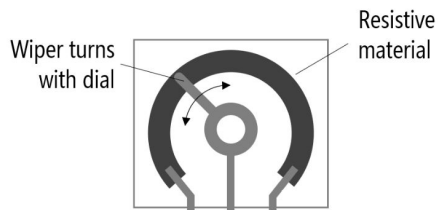

Wiper contact

SCHEMATIC SYMBOL



Wiper contact

Potentiometer

Diodes

Gunn Diode



Laser Diode



Tunnel Diode



LED



Photo Diode



Varactor Diode



PIN Diode



Shockley Diode



Schottky Diode





Step Recovery Diode



Zener Diode




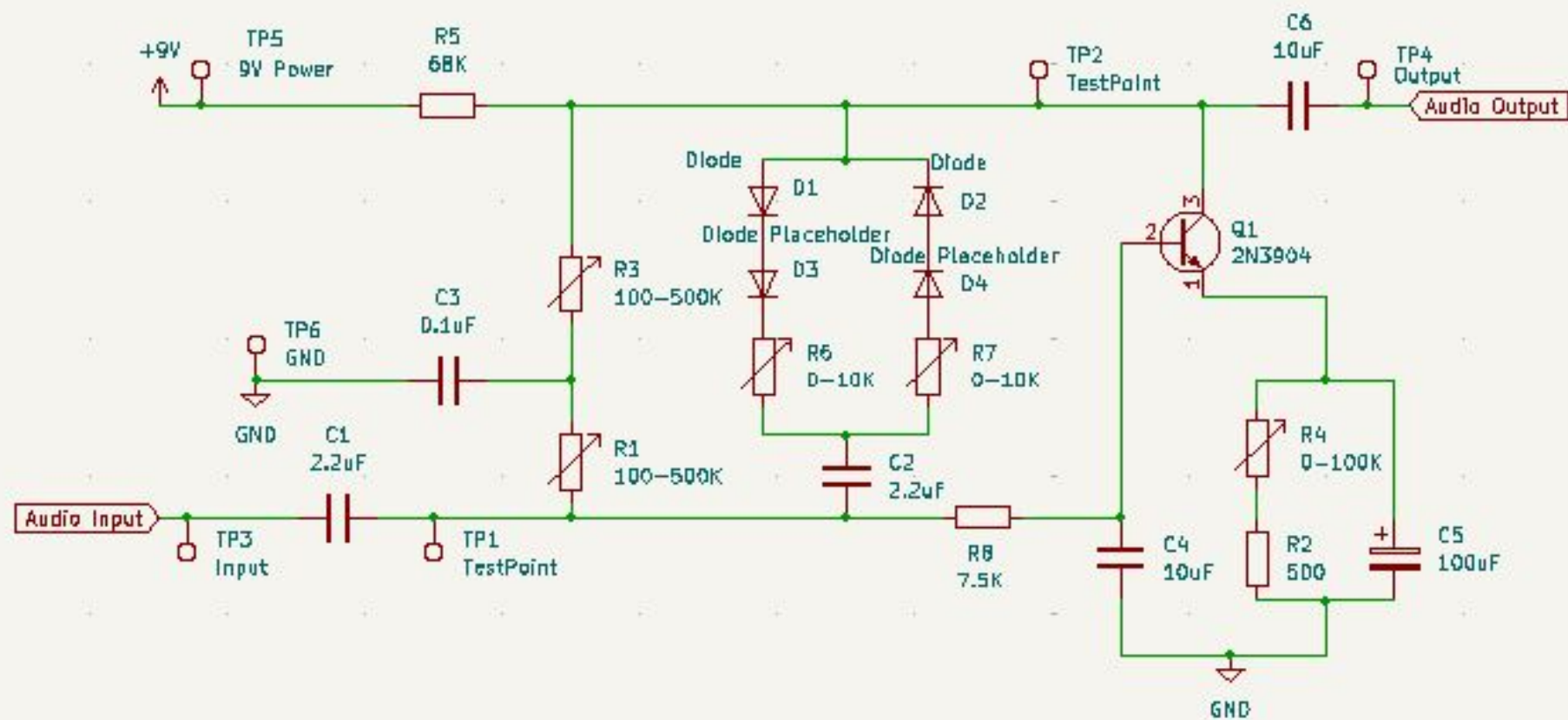

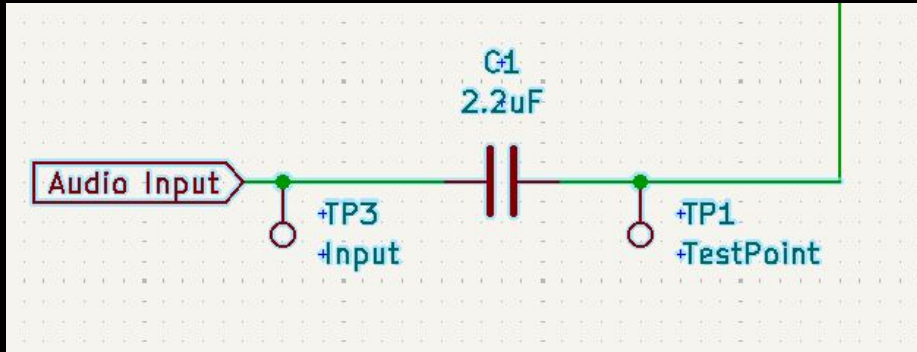

- ❑ The input is a small AC voltage signal with a frequency of **60Hz - 250Hz**
- ❑ High pass filter → why include it and how does this work?
- ❑ Test points → why are these important?


Part 1: Input

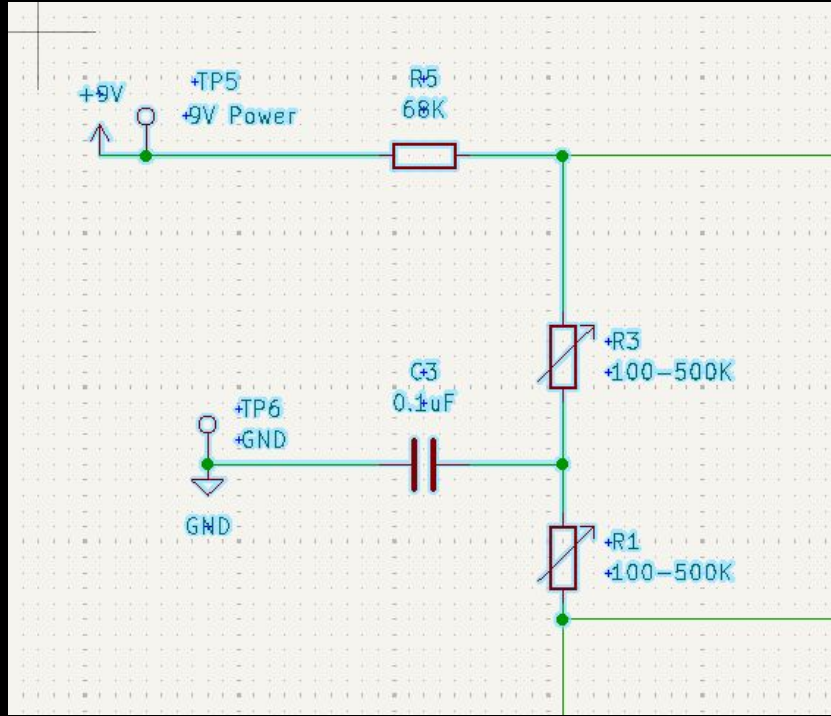

- ❑ **R5** → Connects 9V to the R3, R1 junction, forming a voltage divider that sets the DC offset for the base of the transistor
- ❑ **R3, R1** → Adjustable voltage divider
- ❑ **C3** → Used for AC coupling (ensures DC bias is stable by shunting AC noise signals)

Part 2: DC Offset + Bias


- ❑ **Left branch** → Clips positive values of signal (AC) waveform
- ❑ **Right branch** → Clips negative values of signal (AC) waveform
 - ❑ ↑ diodes = ↑ voltage threshold = ↓ clipping
 - ❑ Adjustable resistor → sloped clipping
- ❑ **C2** → AC coupling
 - Blocks DC signal from clipping branches
 - Passes AC signal to base of the transistor
 - Ensures DC signals from clipping branches don't affect bias voltage divider from previous stage

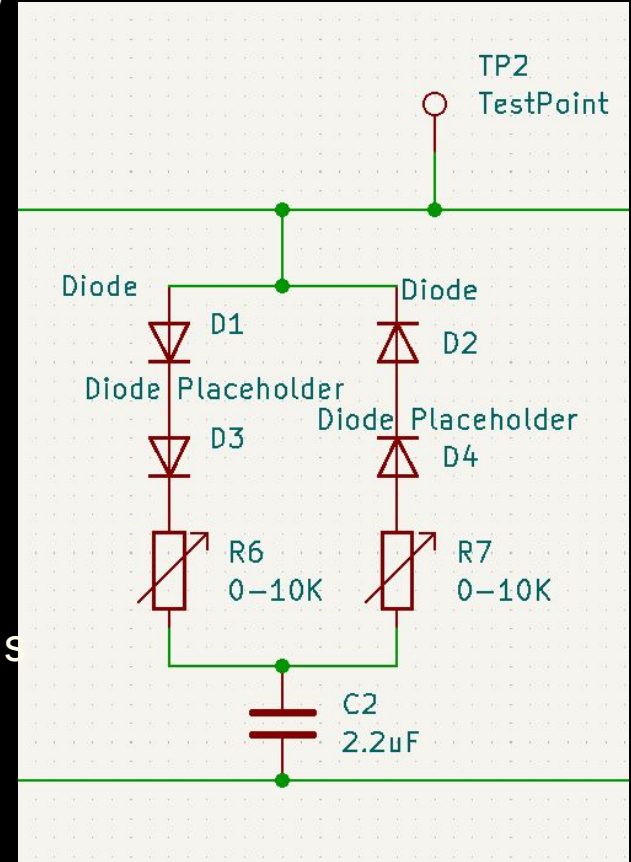

Part 3: Clipping

- ❑ **Transistor** → Biased in active region, it acts as an amplifier
 - Amplifies AC signal on **base**
- ❑ **R8** → Limits base current going into Q1 (protection: think bass guitar) and, with C2, creates a low-pass filter
- ❑ **Negative feedback loop:**
 - ❑ C4 → ↑ signal frequency = ↑ shunted to ground = ↓ gets amplified
 - ❑ R4, R2 → ↓ voltage drop across transistor ($V=IR$) = ↓ amplification of signal
 - ❑ C5 → in parallel with R4 + R2...


↑ signal frequency = capacitor → short = ↑ voltage drop across transistor = ↑ amplification

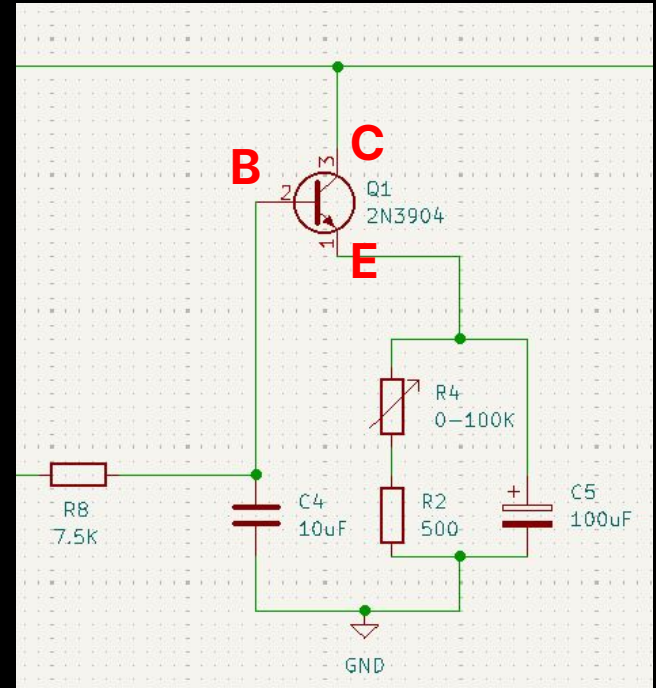


Part 4: Amplification

- ❑ **C6** → AC coupling capacitor that blocks any DC offset present at the collector of the transistor while only passing the amplified AC signal

Think practically: what would happen if it wasn't there?

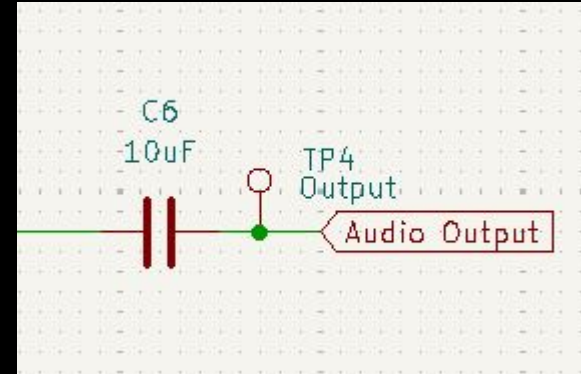

Part 5: Output

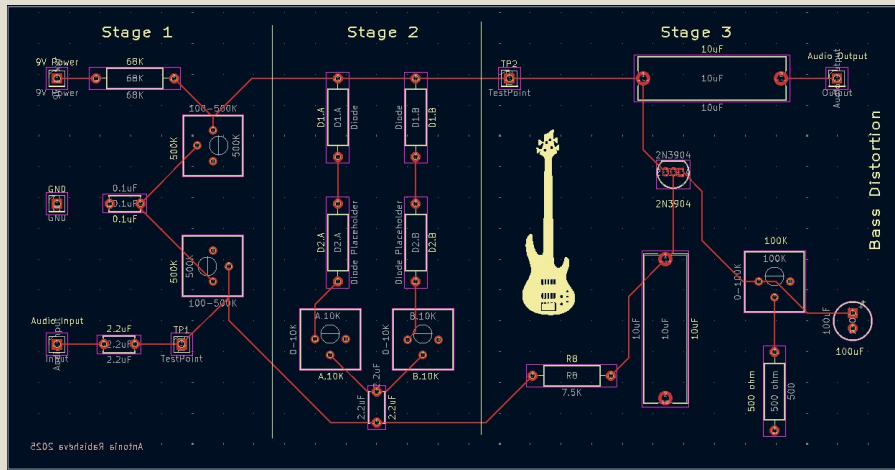

Component List



Name	Quantity	Symbol(s)
2N3904 NPN Transistor	1	Q1
10K pot	2	R6, R7
100K pot	1	R4
500K pot	2	R1, R3
100 uF cap (polarized)	1	C5
2.2uF cap	2	C1, C2
10uF cap	2	C4, C6
0.1 uF capacitors	1	C3
Male/looped pin header	6	TP1 - 6
Female pin header	4	D3 (2), D4 (2)
Resistors	3	R2, R5, R8
Diodes	2	D1, D2

- ❑ **For resistors** → find the indicated value (500 ohm, 68k, 7.5k) in the Hive benchtop drawers
- ❑ **For diodes** → this is part of the distortion you get to personalise! Pick and choose from the Hive benchtop drawers

Fabrication

Simulation/Testing

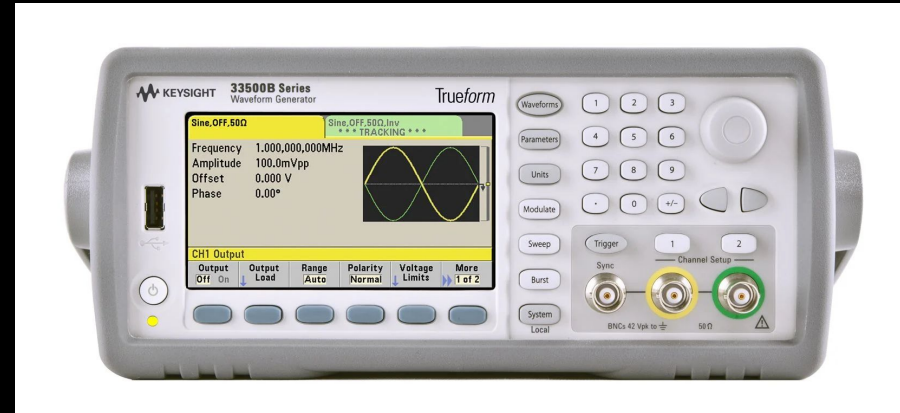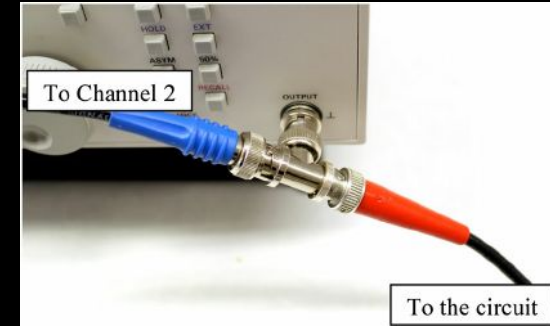
- 1) **Function generator:**
 - a) Use 1 BNC → banana cable and 1 BNC → BNC cable
 - b) Use a **T-splitter** on the input of the generator
 - c) Connect the BNC → BNC cable from the T-splitter to the o-scope input
 - d) Connect other cable from T-splitter to circuit
 - e) Hook up red to input TP
 - f) Hook up black to GND TP
 - g) Set generated function to:
 - i) High-z impedance
 - ii) 100 Hz frequency
 - iii) 1 Vpp amplitude (sine wave)



Simulation/Testing

1) Oscilloscope:

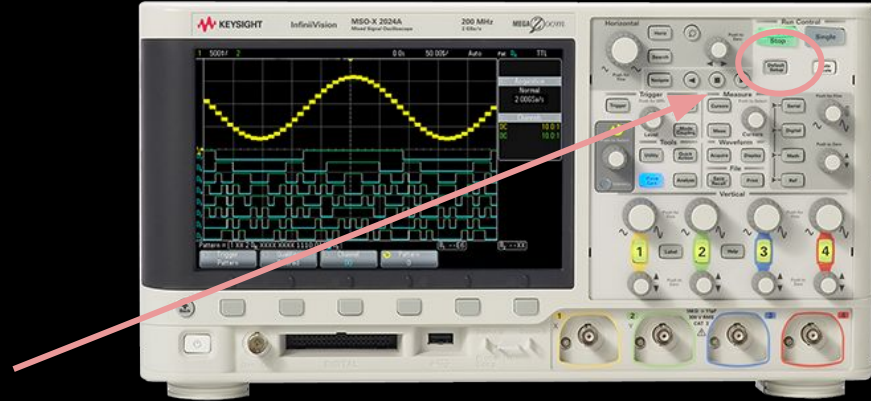- a) Use 1 BNC → banana cable
- b) One input should have the function generator signal
- c) Connect the BNC → banana cable to the other input
- d) Hook up red to output TP
- e) Hook up black to GND TP
- f) Turn on scope and hit **Default Setup**



Simulation/Testing

1) Power Supply:

- a) 2 banana → banana cables
- b) Connect 1 cable from +20V to +9V TP
- c) Connect other cable from COM to GND TP
- d) Set power supply to 9V on the 20V output



What you should expect to see...

For questions/comments on this circuit and workshop, contact:

Antonia (Toni) Rabisheva

~

arabisheva3@gatech.edu

